

Name: \_\_\_\_\_

### **Homework #7: Logic and Circuits (12 points)**

Due to Gradescope by 11:45 PM on Thursday, September 30th

You need to submit a pdf to Gradescope; failure to assign questions to pages will result in a 10% deduction on your grade

Homework Goal: Practice evaluating Boolean expressions, writing truth tables, and following/creating circuits.

#### **Vocab**

1. Practice your vocab from these chapters! (1 point)

We moved away from using vacuum tubes, and now use \_\_\_\_\_, devices that can be ON or OFF, and have no mechanical/moving parts.

Transistors can be combined to create \_\_\_\_\_, which in turn can be combined to create \_\_\_\_\_, which transform a set of binary inputs into a set of binary outputs.

\_\_\_\_\_ is a word used to describe a boolean expression that is never false.

#### **Truth Tables**

2. Provide a truth table for each of the following types of gates: (2 points)
  - a. 2-input NAND gate
  - b. 2-input NOR gate
  - c. 3-input AND gate
  - d. 3-input OR gate


3. Create a truth table for the following Boolean expression: (2 points)  
(b NOR c) OR (NOT b) AND (c NAND a)

### Boolean Logic

4. Assume that  $a = 3$ ,  $b = 5$ ,  $c = 9$ ,  $d = 2$ . What is the result of each of the following Boolean expressions? (2 points)
- $(a > 3) \text{ OR } (b == c)$
  - $[(a + b) > d] \text{ AND } (b < c)$
  - $\text{NOT} [(a == b) \text{ OR } (b == c)]$
  - $(a == 3) \text{ AND } (d == 2) \text{ AND } (c == 7)$

## Circuits

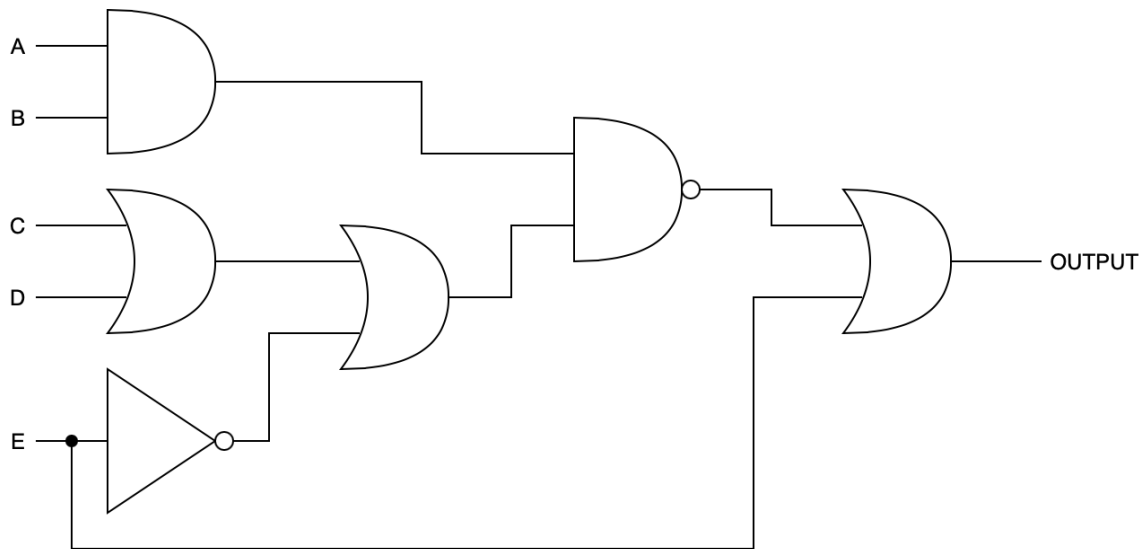5. Given the following circuit diagram, what is the value output when the inputs are  $A = 1$ ,  $B = 0$ ,  $C = 1$ ,  $D = 1$ ,  $E = 0$  (don't miss the two circles in the circuit)? (1 point)



6. Draw the circuit diagram for the following Boolean expression (2 points)  
 $(\text{NOT } a) \text{ AND } (c \text{ OR } (\text{NOT } (b \text{ AND } a)))$

7. Given the following truth table, write a corresponding Boolean expression and then draw the circuit. (2 points)

<b>a</b>	<b>b</b>	<b>c</b>	<b>out</b>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1